

6/4


Unit → 2

AC Circuits

Alternating Voltage & Current

A voltage that varies in both magnitude and polarity with respect to time.

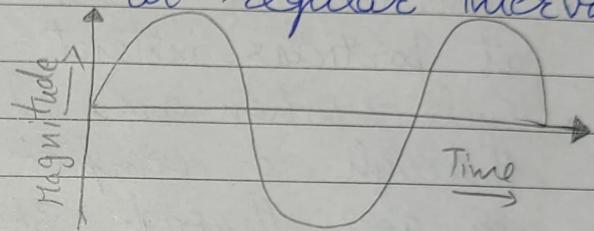A type of electrical current, in which direction of flow of current changes back and forth at regular intervals.




→ Generation of Alternating Voltage and Current.

An Alternating voltage can be generated either by;

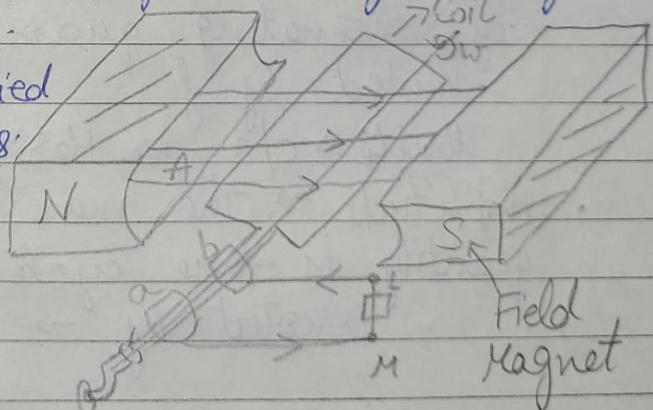
(i) Rotating a coil in uniform magnetic field at constant speed.

It is generally applied in small a.c. generators.



(ii) by rotating a uniform magnetic field within a stationary coil at constant speed.

It is applied in large a.c. generators.

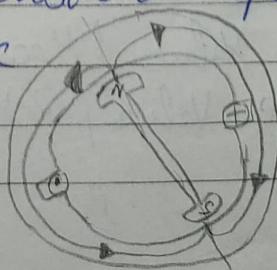

In both the cases; magnetic field is cut by conductors and emf is induced in them.

Important Terms :-

- Wave form \rightarrow The shape of curve obtained by plotting instantaneous values of alternating quantity (voltage or current) along y-axis and time or angle ($\theta = \omega t$) along x-axis.
- Instantaneous Value $\xrightarrow{\text{rel/}}$ The value of an alternating at particular instant of time in the cycle.
- Cycle \rightarrow When an alternating quantity goes through a complete set of +ve and -ve values or goes through 360 electrical degrees; it is said to have completed one cycle.
- Alternation \rightarrow One half cycle.

180 Electrical Degrees.

- Time Period \xrightarrow{T} The time taken in sec to complete one cycle by alternating quantity.
- Frequency \rightarrow Number of cycles made per sec by alternating quantity.
Denoted by f
Units \rightarrow c/s or hertz (Hz).
- Amplitude \rightarrow The max value attained by alternating quantity in one cycle.
Denoted by $\rightarrow E_m (V_m) \rightarrow$ Max value of voltage
 $I_m \rightarrow$ Max value of current.

\Rightarrow Values Of Alternating Voltage and Current

1. Peak Value
2. Average Value / Mean Value
3. Effective Value / R.M.S Value

1: Peak Value \rightarrow The max value attained by alternating quantity during one cycle. This is also called max value | crest value | Amplitude. A Sinusoidal Alternating quantity obtains max value at 90° .

Alternating voltage $\rightarrow E_m$

Alternating Current $\rightarrow I_m$

It is imp in case of testing dielectric strength of insulating materials.

2: Average Value \rightarrow The arithmetic average of all instantaneous values considered of an alternating quantity over one cycle.

Average Value over a complete cycle is zero.

\rightarrow Average Value of Sinusoidal current.

$$i = I_m \sin \theta$$

$$\theta = wt ; I_m = \text{constant}$$

$$I = I_0 \sin wt$$

$$I_{av} = \frac{I}{T} = \frac{q}{T}$$

$$dq = I \cdot dt$$


$$T^{1/2} \int dq = T^{1/2} \int I_0 \sin wt dt$$

$$q = I_0 \left[-\frac{\cos wt}{w} \right]_0^{T/2}$$

$$q = -\frac{I_0}{2\pi/T} \left[\cos \frac{2\pi t}{T} \right]_0^{T/2}$$

$$q = -\frac{I_0 T}{2\pi} [\cos 0 - \cos \pi]$$
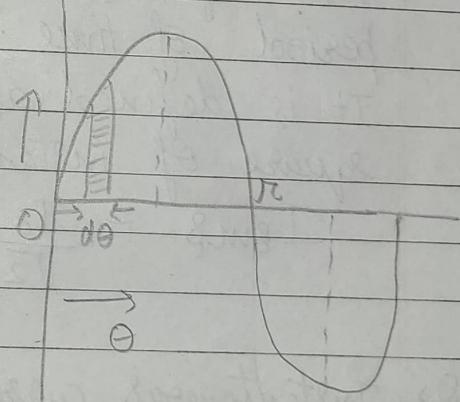
$$q = -\frac{I_0 T}{2\pi} [-1 - 1] = \frac{I_0 T}{\pi}$$



$$I_{av} = \frac{q}{t}$$

$$= \frac{I_0 T}{\pi t}$$

$$[t \rightarrow T/2]$$

$$\Rightarrow \frac{2 I_0 T}{\pi T}$$

$$I_{av} \Rightarrow \frac{2 I_0}{\pi}$$

$$I_{av} = 0.637 I_0$$

#

3. Effective / R.M.S value \rightarrow The steady current, which when flows through a resistor of known resistance for a given period of time than as a result the same quantity of heat is produced by alternating current when flows through same resistor for same period of time.

It is defined as square root of mean of square of instantaneous values.

$$I_{rms} = \frac{I_0}{\sqrt{2}} = 0.707 I_0$$

Q \rightarrow The instantaneous current is given by;

$i = 20 \sin 314t$. Find rms and average value of a.c.

Sol \rightarrow $I = I_0 \sin \omega t$

$$I_0 = 20 A$$

$$\omega = 314$$

$$\begin{aligned} I_{rms} &\Rightarrow I_0 (0.707) \\ &= 20 (0.707) \\ &= 14.14 A \end{aligned}$$

$$I_{av} = 0.637 I_0$$

$$= 0.637 (20)$$

$$= 12.74 A$$

Q → Equation is $I = 42.42 \sin 628t$
Determine.

- (i) Max value (ii) Frequency (iii) RMS value (iv) Average value (v) Form Factor.

Sol → $I = I_0 \sin \omega t$

$$I = 42.42 \sin 628t$$

$$I_0 = 42.42 A$$

$$\omega = 628 \text{ rad/sec}$$

(i) Max value = $I_0 = [42.42 A]$

(ii) Frequency (f)

$$\omega = 2\pi f$$

$$f = \frac{\omega}{2\pi} = \frac{628}{2 \times 3.14} \Rightarrow [314 \text{ Hz}]$$

(iii) RMS value $\Rightarrow I_0 (0.707)$

$$\Rightarrow 42.42 \times 0.707$$

$$\Rightarrow [29.99 A]$$

(iv) Average value $\Rightarrow 0.637 I_0$

$$\Rightarrow 0.637 (42.42)$$

$$\Rightarrow [27.02 A]$$

(v) Form factor $\Rightarrow \frac{I_{rms}}{I_{avg}}$

$$\Rightarrow \frac{29.99}{27.02}$$

$$\Rightarrow [1.10] \#$$

\Rightarrow Formulas

- $I_{rms} = \frac{I_{max}}{\sqrt{2}} \Rightarrow 0.707 I_{max}$

- Form Factor = $\frac{I_{rms}}{I_{avg}} \quad | \quad \frac{E_{rms}}{E_{avg}}$

- Peak Factor = $\frac{I_{max}}{I_{rms}}$


- Average value = $\frac{2}{\pi} I_0 \Rightarrow 0.637 I_0$

- Frequency $\Rightarrow \omega = 2\pi f$

Unit → 2 [Continue ...]
AC Circuits

→ Introduction [Already Done]

Power Triangle

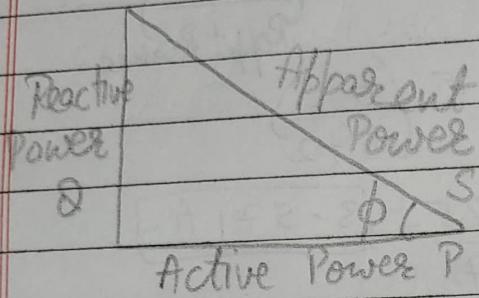

① Active Power

$$P = V_{\text{rms}} I_{\text{rms}} \cdot \cos \phi \quad (\text{Watts})$$

② Apparent Power

$$S = V_{\text{rms}} I_{\text{rms}} \quad (\text{volt - Amp}) \quad (\text{VA})$$

③ Reactive Power

$$Q = V_{\text{rms}} I_{\text{rms}} \sin \phi \quad (\text{volt - Amp - Reactive}) \\ (\text{VAR})$$

$$\phi = 0^\circ$$

$$P = V I$$

{ Using Ohm's law

$$P = I^2 R \quad V = I \cdot R$$

- Power Factor [Unit - less quantity].
- A factor on which entire true power of circuit depends.
 - It is the ratio of active power to apparent power.
 - It is defined as the cosine of the phase difference angle b/w supply voltage and current.

Methods to calculate Power Factor.

$$\textcircled{1} \quad \cos \phi$$

$$\textcircled{2} \quad \cos \phi = \frac{R}{Z}$$

$$\textcircled{3} \quad \cos \phi = \frac{\text{Active Power}}{\text{Apparent Power}}$$

→ Active Power

- It is always positive
- It does not changes its direction
- Power flow is always from source to load.
- Transfers real energy, does work.
- Measured in watts (W).
- Denoted by 'P'.

→ Apparent Power


- Power that is transferred by conductors
- Measured in volt - Amp (V-A).
- Denoted by 'S'.

→ Reactive Power

- It does not do any work.
- Result of current transferring, no energy.
- Measured in VA & s.
- Imaginary part of apparent Power.


Active Power

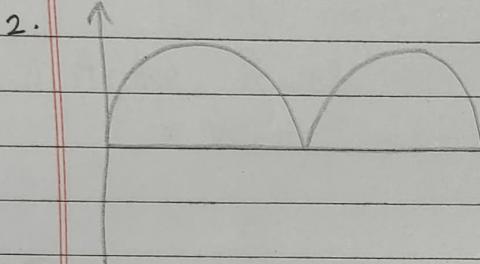1. Real power which is actually utilized in the circuit.



Reactive Power

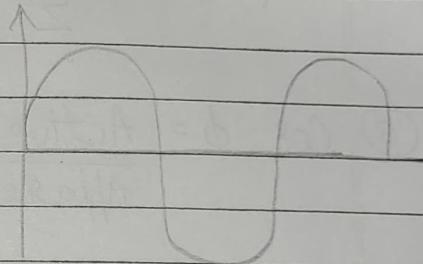- The power which flows back and forth like a pendulum without doing any useful work in circuit.



3. Does not change its direction and remains positive all the time.

Changes its direction periodically and it is positive as well as negative.

Measured using wattmeter.

4. Measured using wattmeter.
5. It produces heat, mechanical power, light, etc.

It only represents power that oscillates back and forth.

6. It is max in purely resistive circuit, and 0 in purely reactive circuit.

It is max in purely reactive circuit, and 0 in purely resistive circuit.

7. It's a function of circuit's dissipative elements, usually resistance.

It's a function of circuit's reactance.

Formula

$$\textcircled{1} \quad \text{Power Factor} (\cos \phi) = \frac{\text{Active Power}}{\text{Apparent Power}} = \frac{kW}{kVA}$$

$$\textcircled{2} \quad P = V I \cos \phi$$

$$I = \frac{P}{V \cos \phi}; \quad \cos \phi = \text{Power Factor}$$

$$\textcircled{3} \quad \text{For } + - = X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$\text{For } \rightarrow \leftarrow = X_L = \omega L = 2\pi f L$$

$$\textcircled{4} \quad \cos \phi = \frac{R}{Z} = \frac{\text{Resistance}}{\text{Impedance}}$$

$$\textcircled{5} \quad Z = \sqrt{R^2 + X^2} = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\textcircled{6} \quad I = I_m \sin \omega t$$

$$\textcircled{7} \quad P \text{ (Active Power)} = V I \cos \theta$$

$$\textcircled{8} \quad Q \text{ (Reactive Power)} = V I \sin \theta$$

$$\textcircled{9} \quad (\text{Apparent Power}) S = \sqrt{P^2 + Q^2}$$

$$\textcircled{10} \quad R = \frac{V}{I}$$

$$Z = \text{Total Resistance}$$

$$= R + X_L + X_C$$

$$Z = \frac{V}{I}; \quad \text{unit } (\Omega).$$

$$\textcircled{11} \quad \tan \phi = \frac{X_L - X_C}{R}$$

$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

(12) $P = VI \cos \phi$

$$VI = \frac{P}{\cos \phi}$$

$$KVA = \frac{KW}{\cos \phi}$$

Numericals

Q) A series circuit consists of a 250Ω non-inductive resistor, a $3H$ inductor of negligible resistance, a $8.5\mu F$ capacitor of negligible resistance. If voltage is $240V$ at 50 Hz . Calculate (i) circuit current (ii) circuit P.F.

Sol - $R = 250\Omega$; $L = 3H$; $C = 8.5\mu F$; $V = 240V$

$$f = 50\text{ Hz}$$

(i). $I = \frac{V}{R}$

$$= \frac{V}{Z}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{250^2 + (942 - 374.67)^2} \\ = 619.97\Omega$$

$$I = \frac{240}{619.97} = 0.387\text{ A}$$

(ii) Power Factor $\Rightarrow \cos \phi$

$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

$$= \tan^{-1} \frac{942 - 374.67}{250}$$

$$= 66.22^\circ$$

$$P.F = \cos \phi = \cos 66.22^\circ \\ = 0.403 \text{ (lagging)}$$

Q) If an inductive coil is connected to a DC supply at 240 V, the current in coil is 15 A. When same coil is connected to an ac supply at 230 V, 50 Hz, the current is 14 A. (a). Calculate;

- (i). resistance, (ii) Impedance, (iii) Reactance,
- (iv). Inductance (v) P.F of coil
- (b). If supply frequency is to be altered to 60 Hz at 240 V; find current in circuit.

Sol. (a) (i) $R = \frac{V}{I} = \frac{240}{15} = [16 \Omega]$

(ii). $Z_L = \frac{V}{I} = \frac{240}{14} = [17.14 \Omega]$

(iii). Reactance $X_L = \sqrt{Z_L^2 - R^2}$
 $= \sqrt{(17.14)^2 - (16)^2}$
 $= [6.14 \Omega]$

(iv). Inductance.

$$L = \frac{X_L}{\omega} = \frac{X_L}{2\pi f} = \frac{6.14}{2 \times 3.14 \times 50} = [19.57 \text{ mH}]$$

(v) P.F

$$\cos \phi = \frac{R}{Z_L} = \frac{16}{17.14} = [0.933]$$

(6). $X_L = 2\pi f L$
 $= 2 \times 3.14 \times 60 \times 19.55 \times 10^{-3}$
 $= 7.366 \Omega$

$$Z_L = \sqrt{R^2 + X_L^2} = \sqrt{16^2 + (7.366)^2} = 17.614 \Omega$$

$$I = \frac{V}{Z_L} = \frac{240}{17.614} = [13.62 \text{ A}]$$